

1. Open circuit	C	A. Slows down the flow of electricity.	<p>Match the electrical component with the water component and diagram symbol</p> <table border="1"> <tr> <td>1. Valve</td> <td>C</td> <td>A. Resistor</td> <td rowspan="6"> </td> </tr> <tr> <td>2. Closed circuit</td> <td>B</td> <td>B. A short-hand way of drawing electrical circuits.</td> </tr> <tr> <td>3. Circuit diagram</td> <td>B</td> <td>C. A circuit with a break in it; no electricity will flow.</td> </tr> <tr> <td>4. Voltage</td> <td>D</td> <td>D. Pushes electricity through a circuit.</td> </tr> <tr> <td>5. Current</td> <td>F</td> <td>E. Electricity can flow through this.</td> </tr> <tr> <td>6. Resistance</td> <td>A</td> <td>F. The flow of electricity through a circuit.</td> </tr> </table>	1. Valve	C	A. Resistor		2. Closed circuit	B	B. A short-hand way of drawing electrical circuits.	3. Circuit diagram	B	C. A circuit with a break in it; no electricity will flow.	4. Voltage	D	D. Pushes electricity through a circuit.	5. Current	F	E. Electricity can flow through this.	6. Resistance	A	F. The flow of electricity through a circuit.
1. Valve	C	A. Resistor																				
2. Closed circuit	B	B. A short-hand way of drawing electrical circuits.																				
3. Circuit diagram	B	C. A circuit with a break in it; no electricity will flow.																				
4. Voltage	D	D. Pushes electricity through a circuit.																				
5. Current	F	E. Electricity can flow through this.																				
6. Resistance	A	F. The flow of electricity through a circuit.																				

Which of the following are correct?

A. B. C. D.

1. Wires	D	A. Used to create radiant energy.
2. Battery	B	B. Pushes electricity through the circuit.
3. Resistor	E	C. Can turn the electricity on and off.
4. Light bulb	A	D. Allows electricity to flow.
5. Switch	C	E. Slows down the flow of electricity.


Label the diagram:

Do all of the light bulbs light up? **NO**

Why or why not?
#3 is short circuited

In the Lab

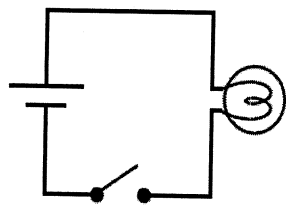
1) Build the following circuit, being sure to connect all components (parts) with wires. Make sure it works.



- Reverse the direction of the battery. Does the light still work?
- Remove the switch. Touch the two wires between the light bulb and battery together to be sure the light still turns on.
- Use these two wires as probes to test which of the following are conductors (C) or insulators (I).

Paper _____	Plastic _____	Water _____
A Penny _____	Cloth _____	Salt Water _____
Paperclip _____	Wood _____	Sugar Water _____
Glass _____	A Dime _____	Rubber _____

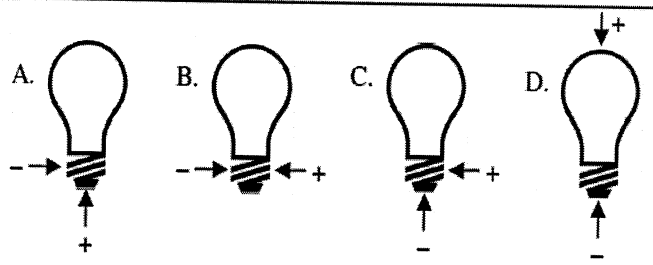Using only a battery, two wires, and a light bulb (no holder), make the light bulb light. Which of the following diagrams will light up the light bulb?



What two parts of a light bulb must be touched to make the light bulb light up?

When the light bulb lights up, is this a closed or open circuit?

What does this mean about the inside of the light bulb?

When the light bulb lights up, what types of energy are used and created?