

- Voltage **D** ~~A~~ Units for voltage. \*
- Current **F** ~~B~~ Restricts electricity flowing in a circuit.
- Resistance **B** ~~C~~ Units for current.
- Amps **C** ~~D~~ Pushes electrons thru a circuit.
- Ohms ( $\Omega$ ) **E** ~~E~~ Units for Resistance.
- Volts **A** ~~R~~ Amount of electricity flowing in a circuit.

- Voltage (V), Current (I), or Resistance (R)? \*
- |   |   |
|---|---|
| A) <b>I</b> Flowing electrons.              | H) <b>R</b> Restricts the flow of current.    |
| B) <b>V</b> Pushes electricity in circuits. | D) <b>V</b> Does work in an electric circuit. |
| C) <b>V</b> Like a water pump.              | J) <b>V</b> Gives electric energy.            |
| D) <b>R</b> Measured in Ohms.               | K) <b>R</b> 12 ohms                           |
| E) <b>I</b> Measured in Amps.               | L) <b>V</b> 36 volts.                         |
| F) <b>V</b> A battery gives this.           | M) <b>I</b> 5 amps.                           |
| G) <b>V</b> Measured in volts.              |   |

Which has more current flowing thru it? \*

A **loud** radio or a quiet radio?

A dim light bulb or a **bright** light bulb?

A **fast** toy car or a slow toy car?

A cold wire or a **hot** wire?

Which will have more resistance: an **insulator** or a conductor?

Which resistor is the better conductor: **150 $\Omega$**  or 600 $\Omega$ ?

Which resistor is the better insulator: **240 $\Omega$**  or 6 $\Omega$ ?



- Voltage (V), Current (I), or Resistance (R)? \*
- I** If you increase resistance what decreases?
  - I** If you increases voltage what increases?  $I = \frac{V}{R}$
  - R** If the current decreased what increased?
  - V** If current increased what increased?
  - R** If current increased what decreased?
  - I** If resistance is decreased, what increases?
  - V, I** More batteries will increase these two quantities.

How much current does a 9V battery push thru a 3 $\Omega$  resistor? \*

Given	Equation	Rearrange	Calculate
$V = 9V$ $R = 3\Omega$	$I = \frac{V}{R}$	$I = \frac{9V}{3\Omega}$	$I = 3A$

A 4  $\Omega$  resistor has 3A running thru it. Find the battery's voltage.

Given	Equation	Rearrange	Calculate
$I = 3A$ $R = 4\Omega$	$V = I \cdot R$	$V = 3A \cdot 4\Omega$	$V = 12V$

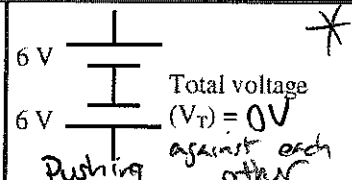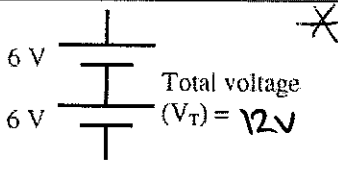

An 18V battery produces 2A in the circuit. How much resistance is in the circuit?

Given	Equation	Rearrange	Calculate
$V = 18V$ $I = 2A$	$R = \frac{V}{I}$	$R = \frac{18V}{2A}$	$R = 9\Omega$


When the switch is closed will the light turn on? **No**  
Why or why not?  
**Batteries are opposing each other**

Which of these two water towers would give the most voltage to a water circuit?

Add (A) or reduce (R) voltage?  
Resistors? **R** Wires? **no change** Batteries? **A**

Which light bulbs will light? (All are in closed circuits.)  
If it does light, draw an arrow to show the direction of current.

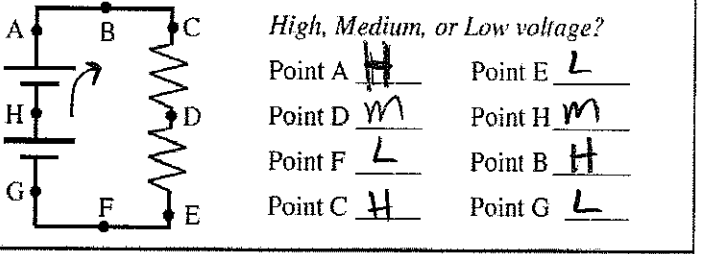3V **No** 3V  
6V **Yes** 3V  
9V **Yes** 0V  
9V **No** 9V



With the same resistance, which battery will cause more current to flow: a 12V or a **24V** battery?

Voltage give what kind of energy to electricity?  
**PE**

How much potential energy does water have after it falls to the ground?  
**0J**

How much voltage does a circuit have just before going back thru the batteries?  
**0J**

A bird lands on a 20,000 volt wire. Both feet are touching.

- What voltage is the bird's left foot? **20,000V**
- What voltage is the bird's right foot? **20,000V**
- What is the *difference of voltage* between the bird's feet?  
**0V**
- So, why can a bird land on an electrical wire and not get electrocuted?  
**no voltage difference between birds feet**