


- 1. Fuse **B** An independent path in a parallel circuit.
- 2. Circuit breaker **D** A device that breaks to protect against excessive current. Must be replaced.
- 3. Wire **E** Where branches joint or split.
- 4. Branch **A** Protects against high current, but can be reset.
- 5. Power **F** Where most of the electrons in a circuit come from.
- 6. Junction **C** The product of voltage and current.

Which is brighter: a 60 W or a 100 W bulb?
Which one uses more power?
100W

A 4 Ω and a 10 Ω light bulb are in series. Which one is brighter?
Why? **In series - same current, more voltage**

A 4 Ω and a 10 Ω light bulb are in parallel. Which is brighter?
Why? **Same Voltage - 4Ω more current
more Power**


Label the voltages at the letters.

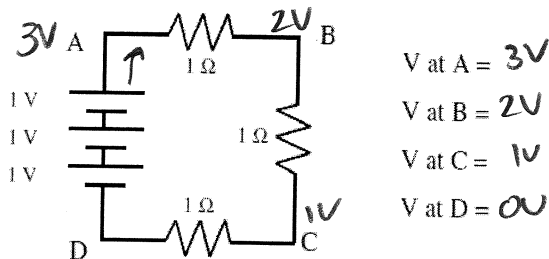

The electricity in your house is 120 volts. How many amps does a 60 watt light bulb use?
**P 60W P = V · I
I ? I = P / V = 60W / 120V = 0.5A**

How much power is used by a 120 V circuit using 6 amps?
**P
I 6A P = V · I
V 120V = 120V · 6A = 720W**

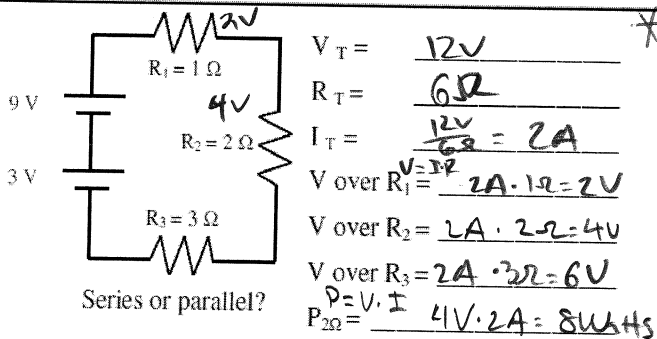A 240 volt circuit (like your dryer) has 20 amps flowing through it. How much power is it using?
**P
V 240V P = VI
I 20A 240V · 20A = 4800 W or 4.8kW**





35 amps of current goes through a 40 amp fuse. What happens?
Nothing

25 amps of current goes through a 15 amp fuse. What happens?
Fuse melts

Which resistor uses the most power? **R3**

Why? **uses most Voltage**

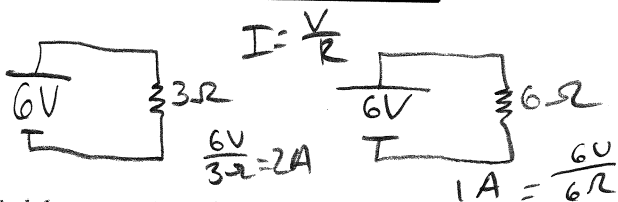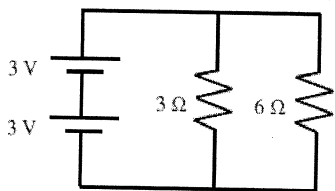
Split the following parallel circuit into two independent series circuits.




Find the current in each circuit.

Find the total current. **3A**

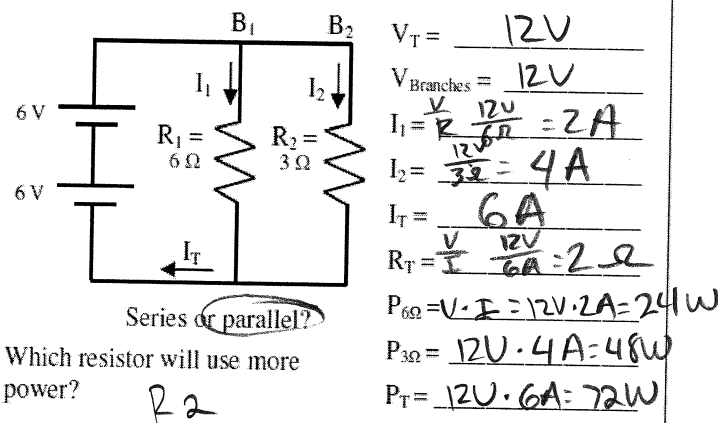Find the total resistance.
 $R_T = \frac{V_T}{I_T} = \frac{6V}{3A} = 2Ω$



Which resistor will use more power?
R2

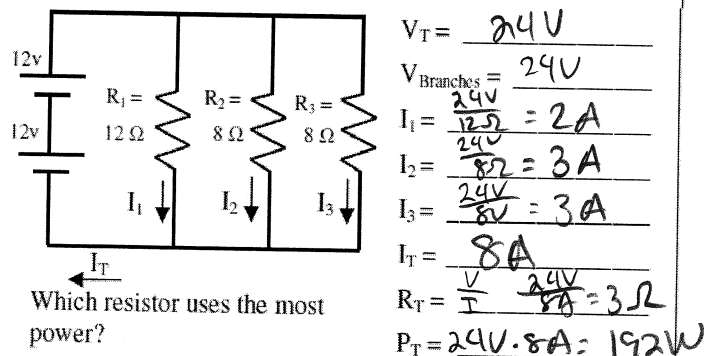

Which resistor uses the most power?