Period:

Electricity and Magnetism Review

- Voltage \bigcirc A. 8 amps = \bigcirc
- Resistance $\mathbb{E}[B. 8 \text{ volts} =]/$
- Power 🗁 C. 8 coulombs $= \bigcirc$
- D. 8 watts = \triangleright Charge C
- Current H E. 8 ohms = 2


What moves: electrons of protons?

Why? protons are stuck in nucleus by strong nuclear force.

An object has a charge of -8 C.

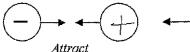- A) Is the object-positive or negative?
- B) Did it gain or lose electrons?
- C) If you touch it to ground, will it lose electrons to ground or gain electrons from ground?
- D) What will its charge be after it is grounded? O

What are the charges of the second objects?





What is electricity? moving

Will electrons flow between the two objects?







Why does electricity move?
There's a diff. of charge

What is arcing? SOOR between two objects

When and why does arcing occur? Jiff, of charge + electric force

If a 12 v battery is connected to a 24 Ω resistor, how much

 $\frac{\text{current is flowing?}}{V=12V} = \frac{V}{R} = \frac{12}{24} = .5A$ D=2452

How much voltage is needed to produce 2 amps through a 4 ohm

light bulb? I== V=2(4)=8V I=2A VIII 2=412

If a light bulb in your house (120 V) draws 0.5 amps, how much power does it use?

P=VI=120(.5) 1/5/201 = 60W T = 15H

- 1. Current
- A. A path for electricity to flow.
- Voltage ==
- B. A material that allows electricity to
- Resistance D
- A material that resists electricity.
- Insulator
- D. Slows down electricity
- Conductor &
- E What pushes electricity in a circuit.
- Circuit
- F. The flow of electrons thru wires.

CONJUCTOR allows electricity or heat to pass through it.

Electricity flows through paths called circuits. A Closed circuit has no breaks in it, while an open circuit has a break and stops the flow of electricity.

An 「ハシリラ† <u>DV</u> will not allow electricity to pass.

Electricity is made up of flowing elect rous

Like electric charges attract/tepel/Opposite charges attract/ repel.

Draw a circuit of two batteries, a light bulb, a resistor, and a switch, all in series.



You have two light bulbs and a battery in a circuit. If you add another battery, do the light bulbs get brighter or dimmer? Why? more 1/= move I

You have two light bulbs and a battery in a circuit. If you add another light bulb, do the light bulbs get brighter of dimmer?

more bulbs = more R = 1055 I

Increases (I) OrDecreases (D) Increasing resistance current Decreasing resistance _ = current Increasing voltage ___ current Decreasing voltage \triangleright current

How can you tell if two light bulbs are in parallel?

unscrew 1, other stays on. How can you tell if two light bulbs are in series?

unscrew 1, both go off.

Is your house wired in series or in parallel? Why?

devices are indep.

Period:

What is the change of voltage across a wire?

Why can a bird sit on a wire and not be electrocuted?

No voltage diffications feet

What happens when you short circuit one light bulb in a two light bulb circuit?


Where do most of the electrons come from that run thru a circuit?

What happens if you short circuit a battery?

Series

parallel?

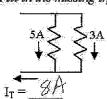Fill in the missing information on the following graphics.








$$6V \frac{\cancel{4}}{\cancel{5}} \checkmark$$

$$3V \frac{\cancel{5}}{\cancel{5}} \checkmark$$

$$V_{T} = \cancel{4} \checkmark$$

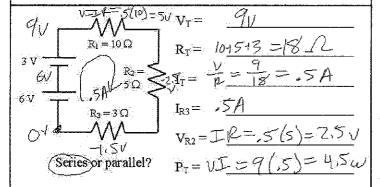

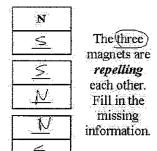

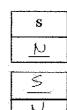

The two magnets are attracting each other. Fill in the missing information.

Someone asks you how what a circuit is and how it works.

circuit is a path for moving es. voltage pushes, current flows, resistance slows it down.

What are fuses and circuit breakers?

Ir= 184/20 = 9A

How are they different?

What will a magnet attract?

Ferras metals + opp. pole of

What will a magnet repel?

some pole magn.

What does moving electricity cause? Magnets

What do moving magnets cause?

What is an electromagnet?

How do you strengthen an electromagnet?

What is a motor?

How does it work?

What is a generator?

How does it work?